

# US03CPHY02

## UNIT 2 Small Signal Amplifiers

### *Part-1*



**Dr. T. H. Patel**  
Associate Professor  
VP & RPTP Science College  
Vallabh Vidyanagar-388120  
Gujarat, India.

<http://pateltarunh.weebly.com>

# US03CPHY02 Unit I & II

## **UNIT- I        Transistor Biasing Circuits**

Introduction, Need to bias a transistor, Selection of operating point, Need for bias stabilization, Requirement of a biasing circuits, Different biasing circuits, Fixed-bias circuit, Collector to base bias circuit, Voltage divider biasing circuit, Approximate analysis, Accurate analysis, Emitter-bias circuit, PNP transistor biasing circuit, Related numericals





## **UNIT- II        Small Signal Amplifiers and h-parameters**

Introduction, Single stage transistor amplifier, Amplifier performance analysis methods, Graphical method, AC and DC load lines, Calculation of gain, Input and output phase relationship, Equivalent circuit method, Development of transistor AC equivalent circuit, h-parameter equivalent circuit, Amplifier analysis, Need of multistage amplifier, Gain of multistage amplifier, Related numericals

# So far you have studied the ....



- Transistor Structure: PNP & NPN
- Transistor Operation modes: CB,CC and CE
- Transistor Characteristics : Input and Output
- Operating Point : ( $I_B$ ,  $I_C$ ,  $V_{CE}$ )
- Biasing Circuits: Fixed Bias, C to B Bias,  
Voltage Divider Biasing & Emitter Bias Circuit.

# Transistor Structure

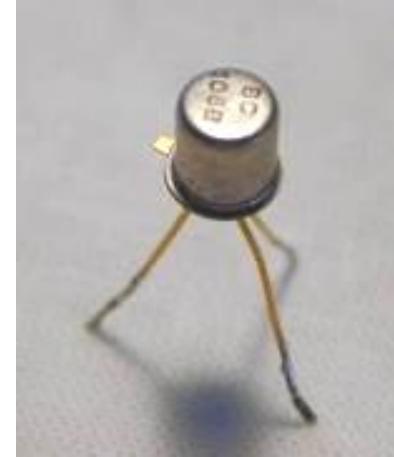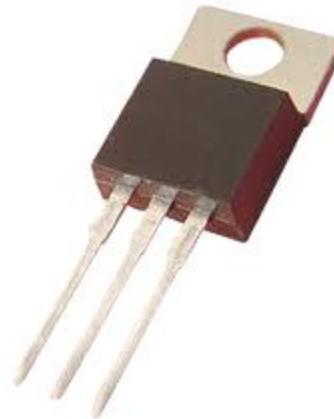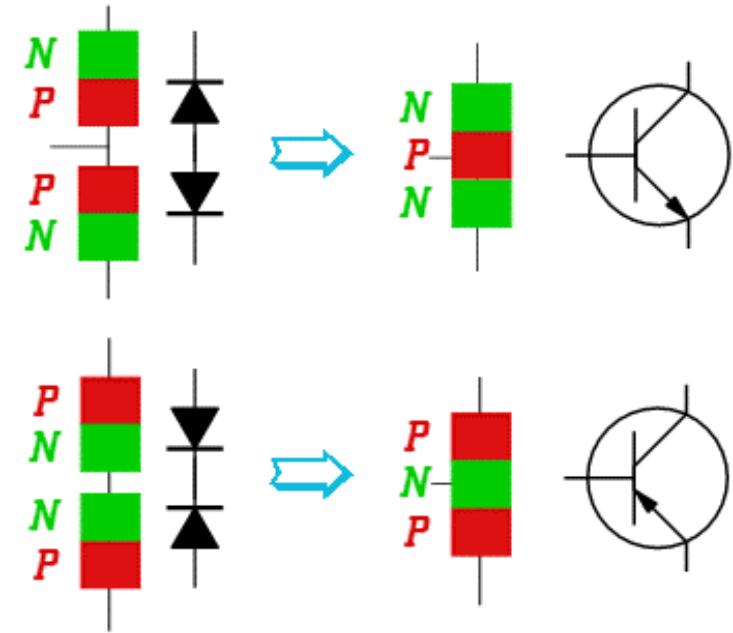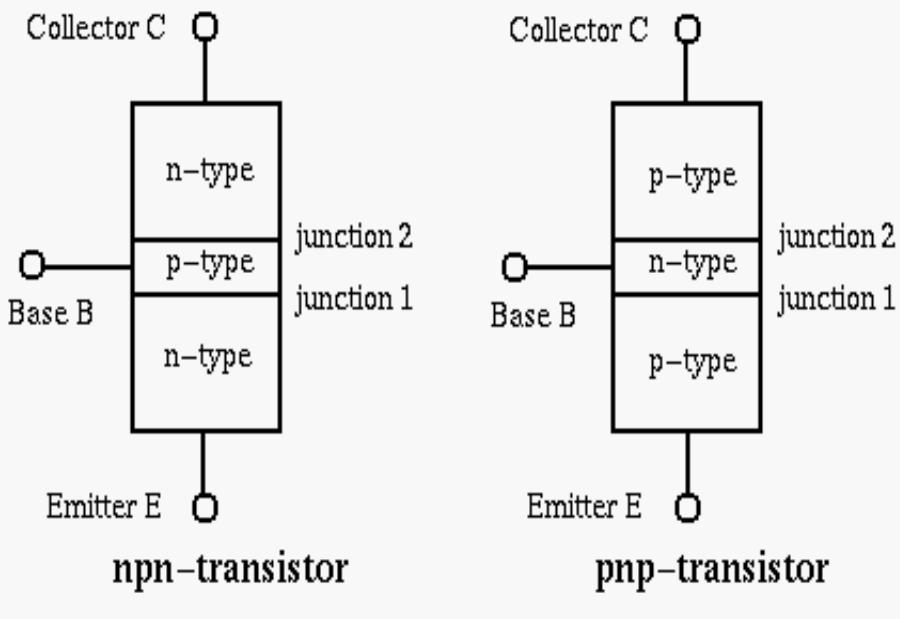


# Transistor Operational Modes

## Common Base (CB)

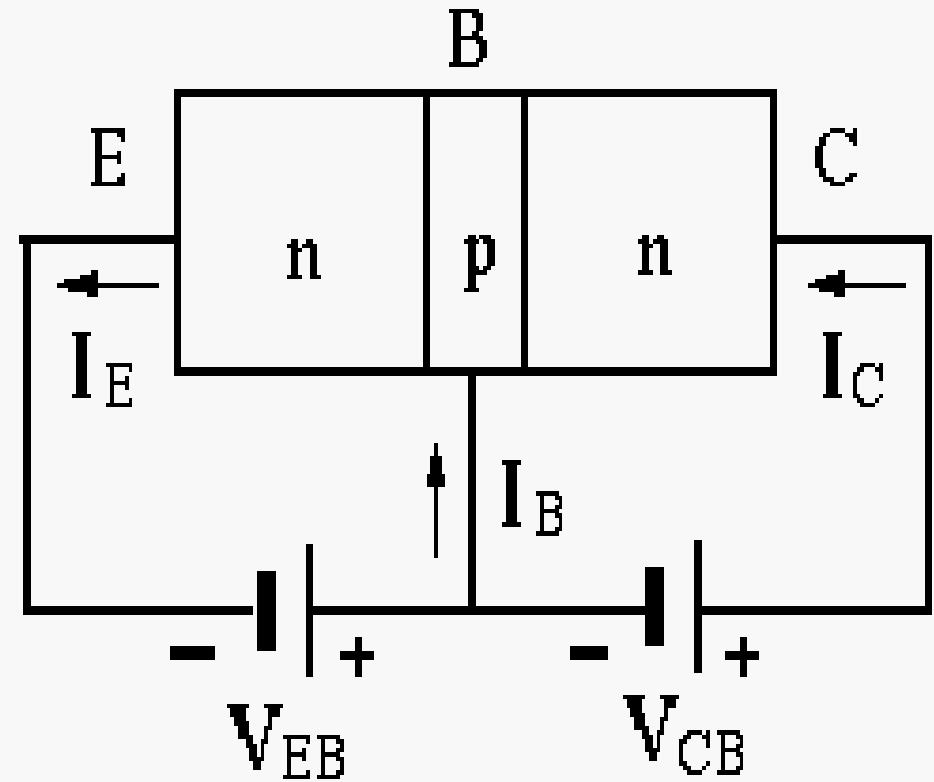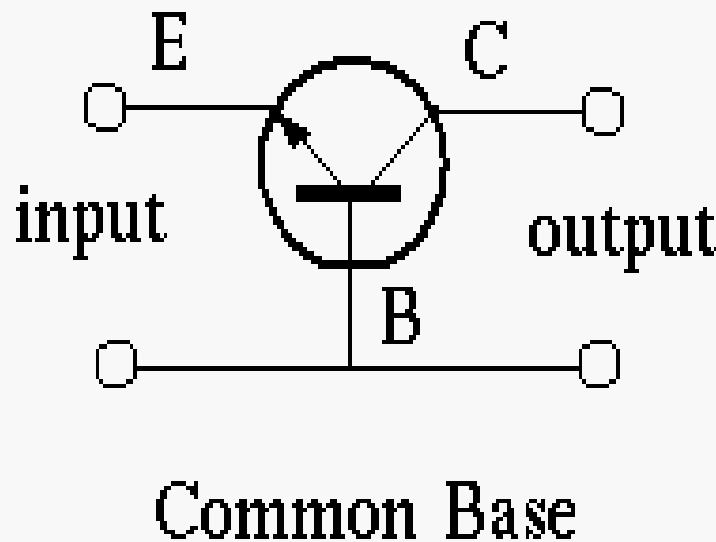


# Transistor Operational Modes

## Common Emitter (CE)

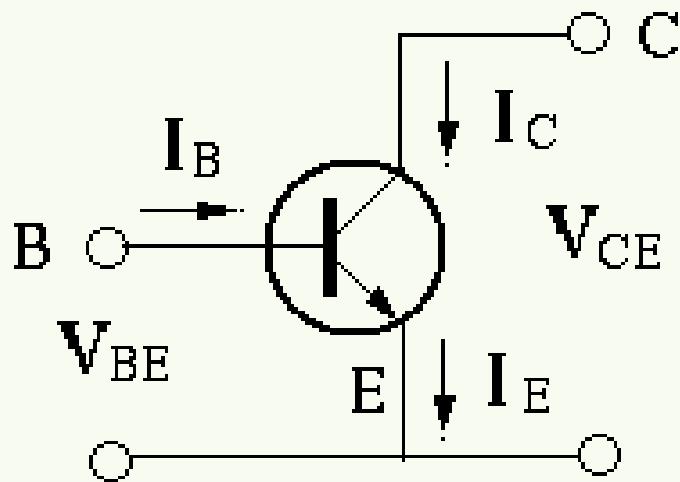


Common Emitter

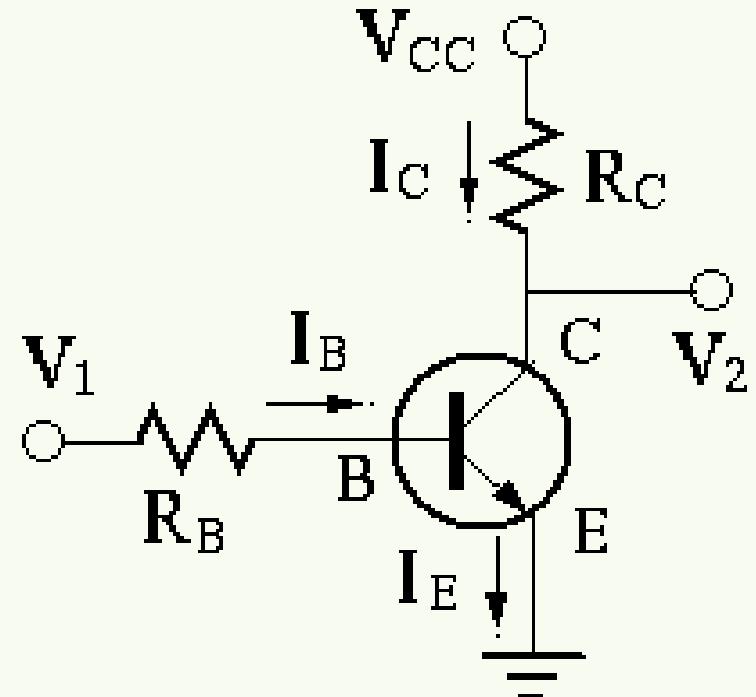


CE Voltage Amplifier

CC Mode – assignment!

# CE Transistor Characteristics




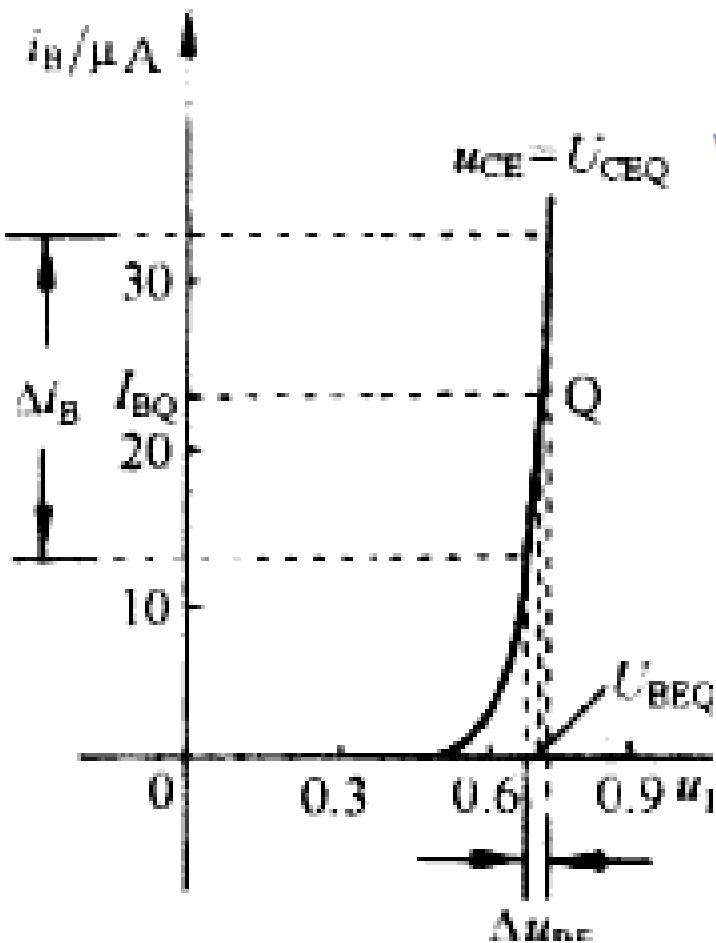


**Input Characteristics**

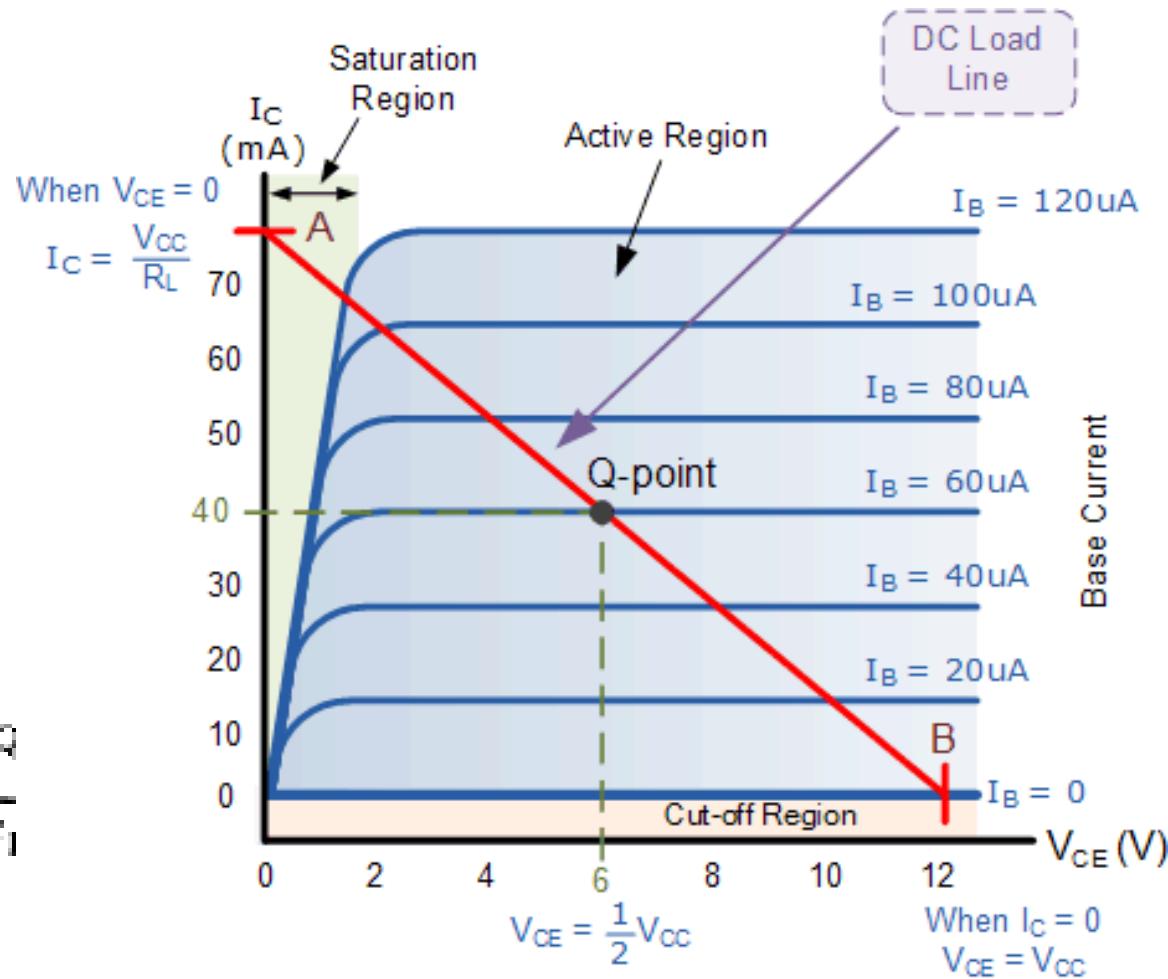

**Output Characteristics**

# Transistor Biasing Circuits

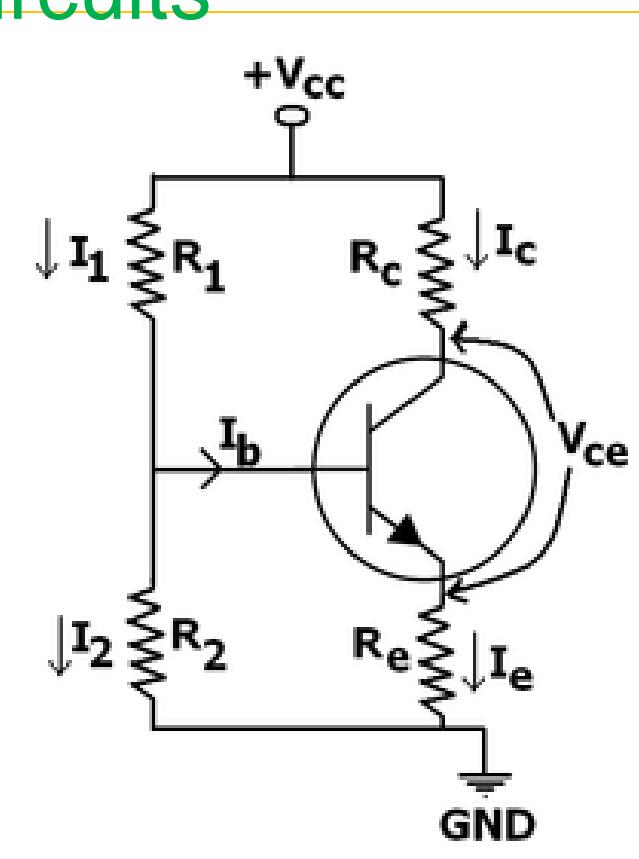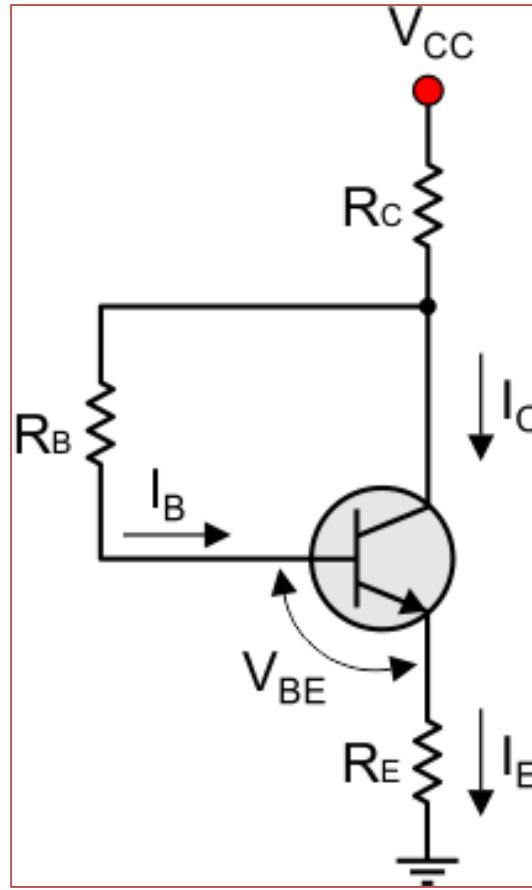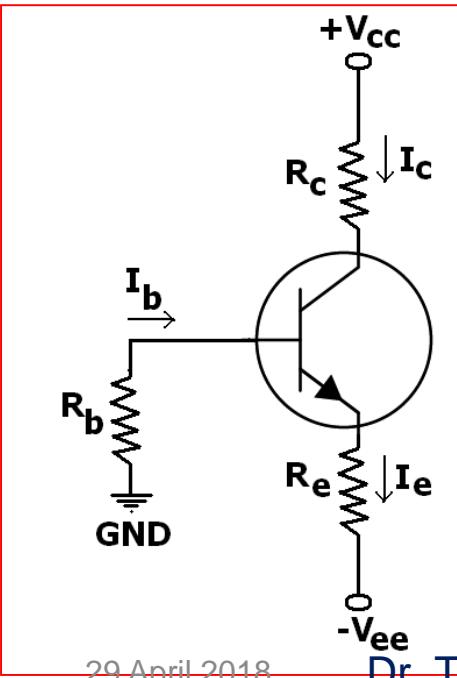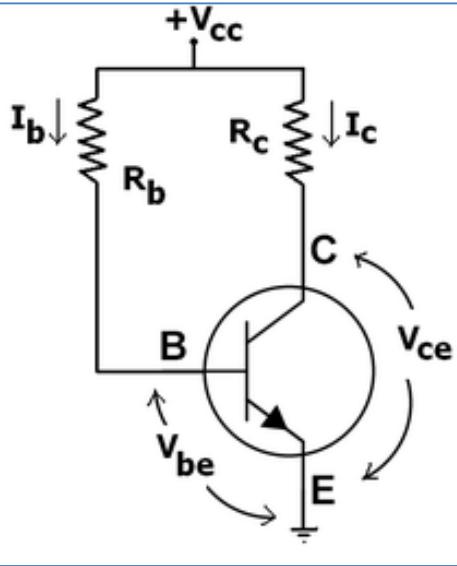

# Now, from here, ahead...

- Small Signal Amplifier
- Graphical Method
- Equivalent Circuit Method
- h-Parameters: Transistor as a Two-Port System
- h-Parameter Equivalent Circuit of a Transistor
- h-Parameter: Determination for CE Transistor
- CE Amplifier: Analysis using h-parameters
- Example:
- Multi-stage Amplifiers

# What are Small Signal Amplifiers ?

When variation of output ( $i_c$ ) with input ( $i_b$ ) are not very large the amplifier is called: *Small Signal Amplifier.*

*Applicatio*

*Radio & T*


*Tap Recor*

*Stereos*

*Measuring instruments*



# Single Stage Transistor Amplifier

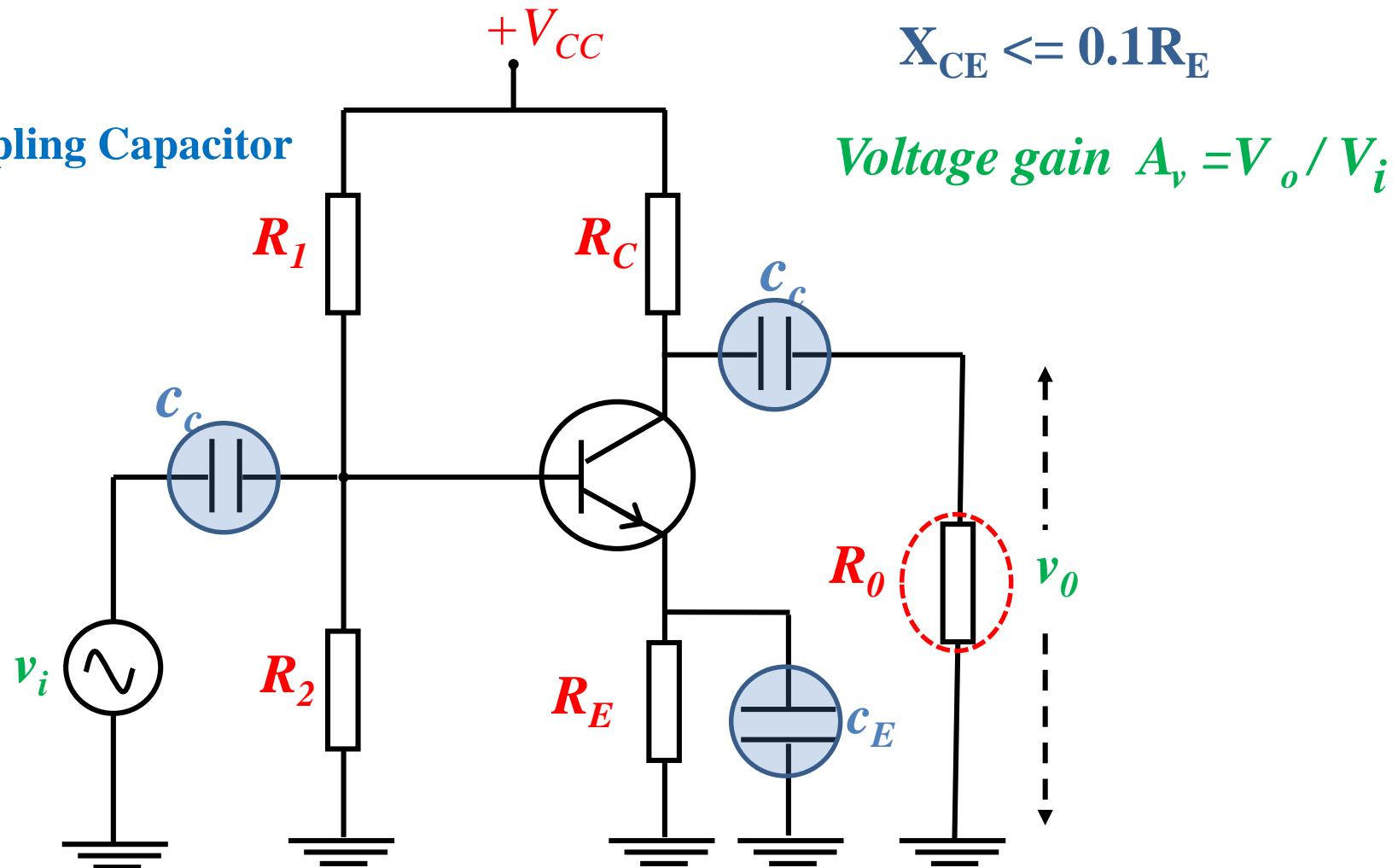

# Small Signal Amplifier Analysis: why ?

The following parameters of amplifier are used to describe the performance of the circuit.

1. Input Impedance ( $Z_i$ )
2. Output Impedance ( $Z_0$ )
3. Current Gain ( $A_i$ )
4. Voltage Gain ( $A_v$ ) and
5. Bandwidth

The transistor circuits needs to be analyzed to determine the values of these parameters.

# Small Signal Amplifier: Analysis


1. Graphical Method.
2. Equivalent Circuit Method.

# Graphical Method for Amplifier Analysis
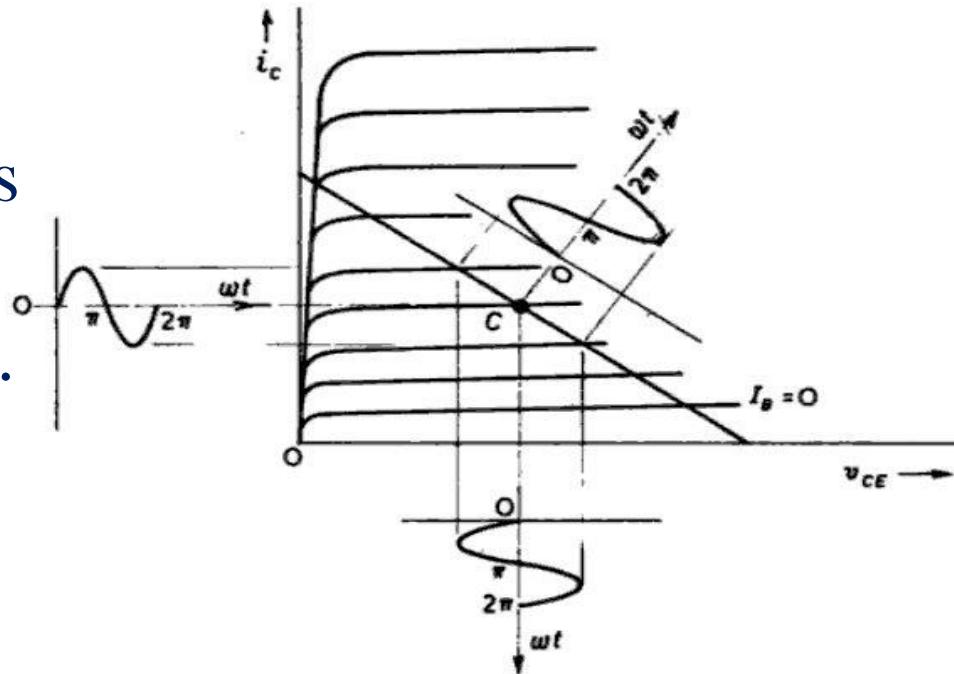
## Advantages:

- No approximate assumptions.
- More accurate results than other methods.
- Only method suitable for large signal amplifiers and power amplifiers.

We need output characteristics supplied by manufacturer to see variations of  $I_B$ ,  $I_C$  and  $V_{CE}$ .




# Graphical Method for Amplifier Analysis

The method involves the determination of;

1. DC Load Line (DC Analysis)
2. AC Load Line (AC Analysis)
3. Current Gain
4. Voltage gain
5. Phase Relations
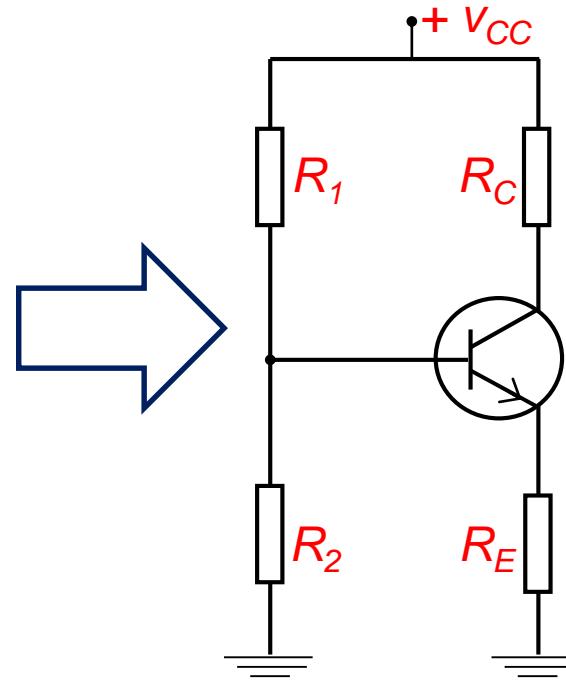
# Graphical Method: DC Analysis (DC Load Line)

*Are DC and AC Load Lines same or different ?*




DC behavior

For all DC currents or voltages all Cs make open circuit.

# Graphical Method: DC Analysis

DC load line:

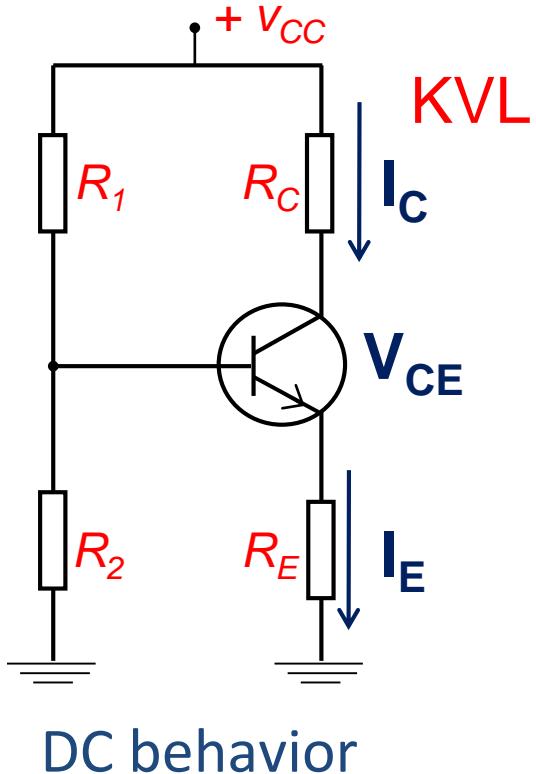

DC behavior

$$V_{cc} = I_C R_C + V_{CE} + I_E R_E$$


$$\therefore V_{cc} = I_C R_C + V_{CE} + I_C R_E$$

$$\therefore I_C = \frac{-1}{(R_C + R_E)} V_{CE} + \frac{V_{CC}}{(R_C + R_E)}$$

$y = mx + c$


When  $V_{CE} = 0$ ,  $I_C = V_{CC} / (R_C + R_E)$  A

When  $I_C = 0$ ,  $V_{CC} = V_{CE}$  B


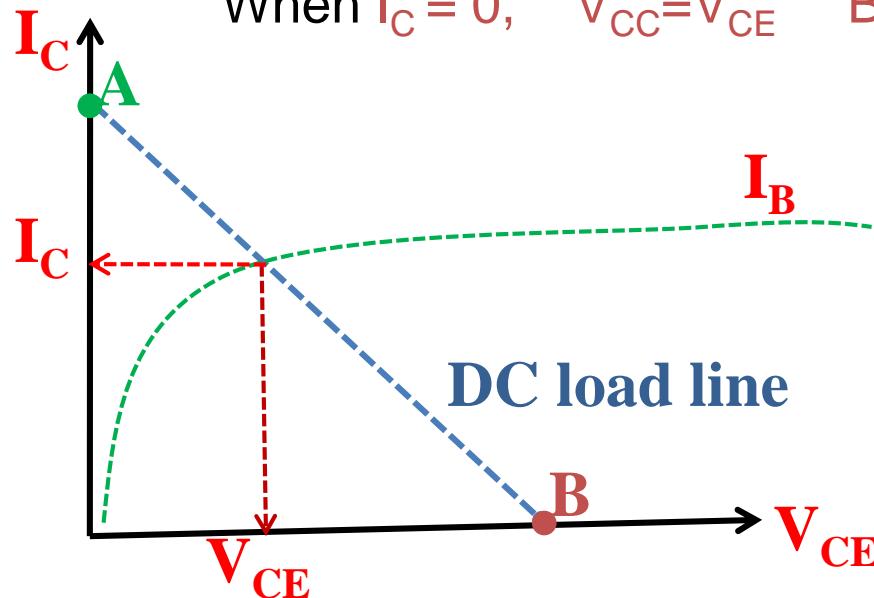


# Graphical Method: DC Analysis
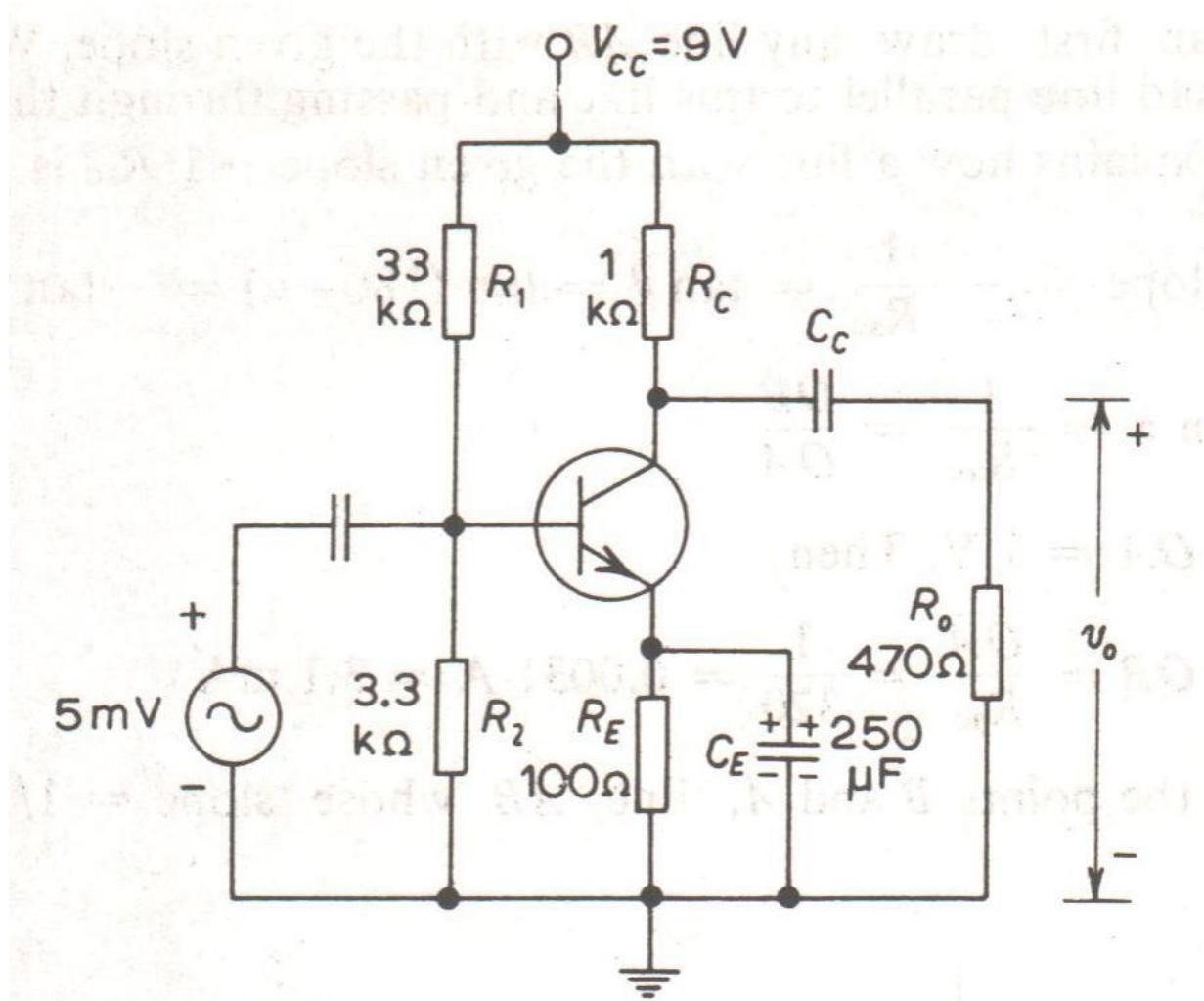
## Determination of DC load line; Example:




# Graphical Method: DC Analysis

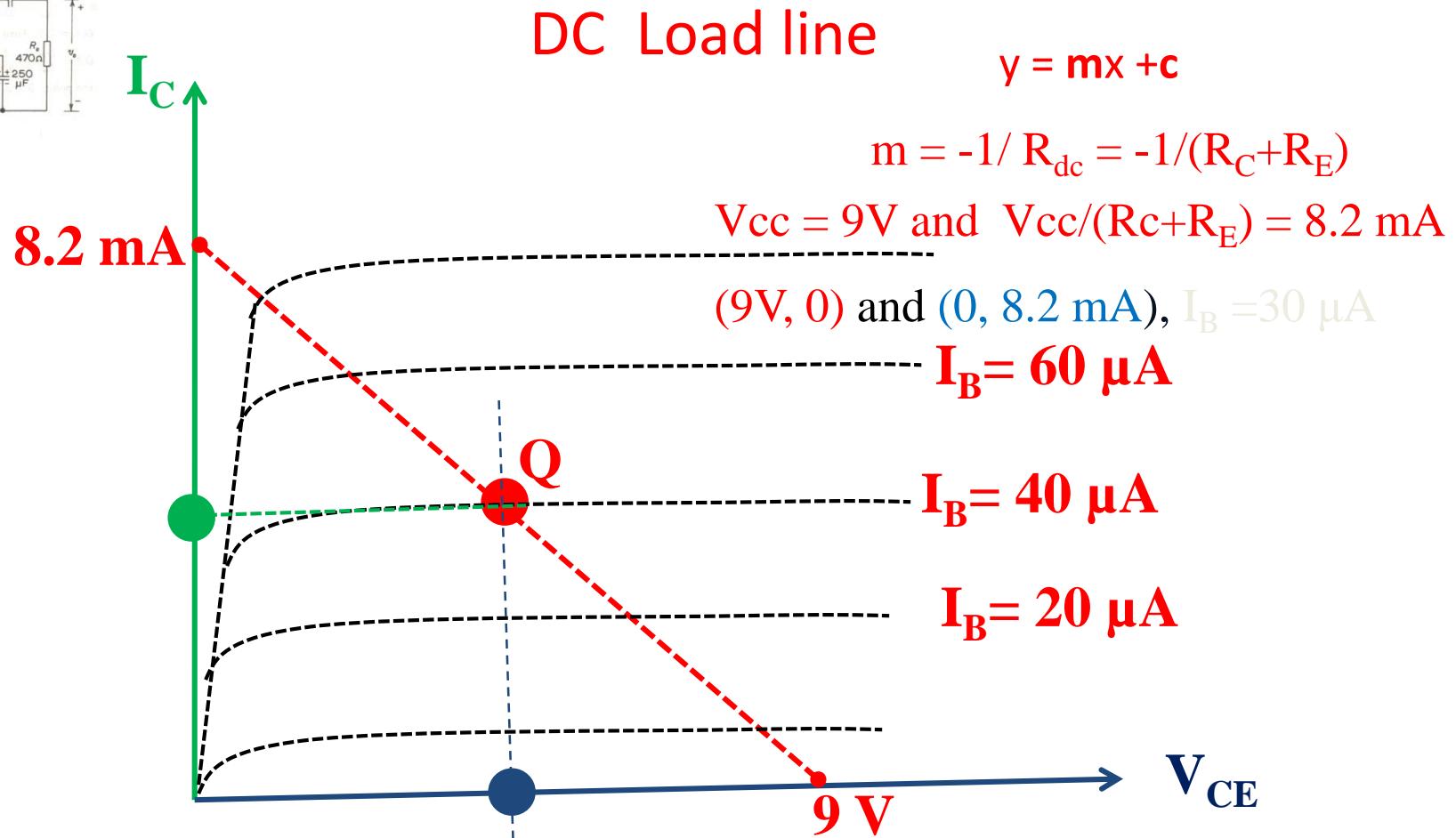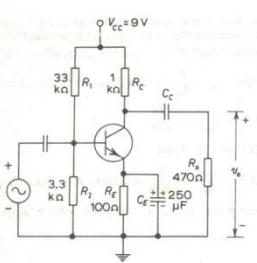

$$\therefore I_C = \frac{-1}{(R_C + R_E)} V_{CE} + \frac{V_{CC}}{(R_C + R_E)}$$

# Graphical Method: DC Analysis
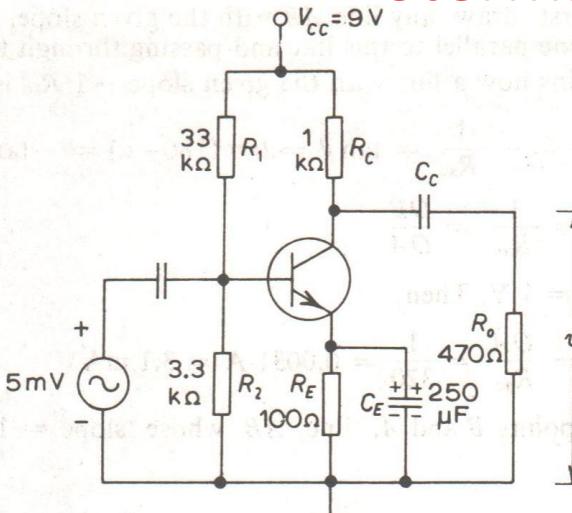
## Determination of DC load line; Example:



$$\therefore I_C = \frac{-1}{(R_C + R_E)} V_{CE} + \frac{V_{CC}}{(R_C + R_E)}$$

**y = mx + c**

$$m = -1/R_{dc} = -1/(R_C + R_E)$$


V<sub>CC</sub> = 9V and

$$V_{CC}/(R_C + R_E) = 8.2 \text{ mA}$$

$$(9V, 0) \text{ and } (0, 8.2 \text{ mA}), I_B = 30 \mu\text{A}$$




29 April 2018

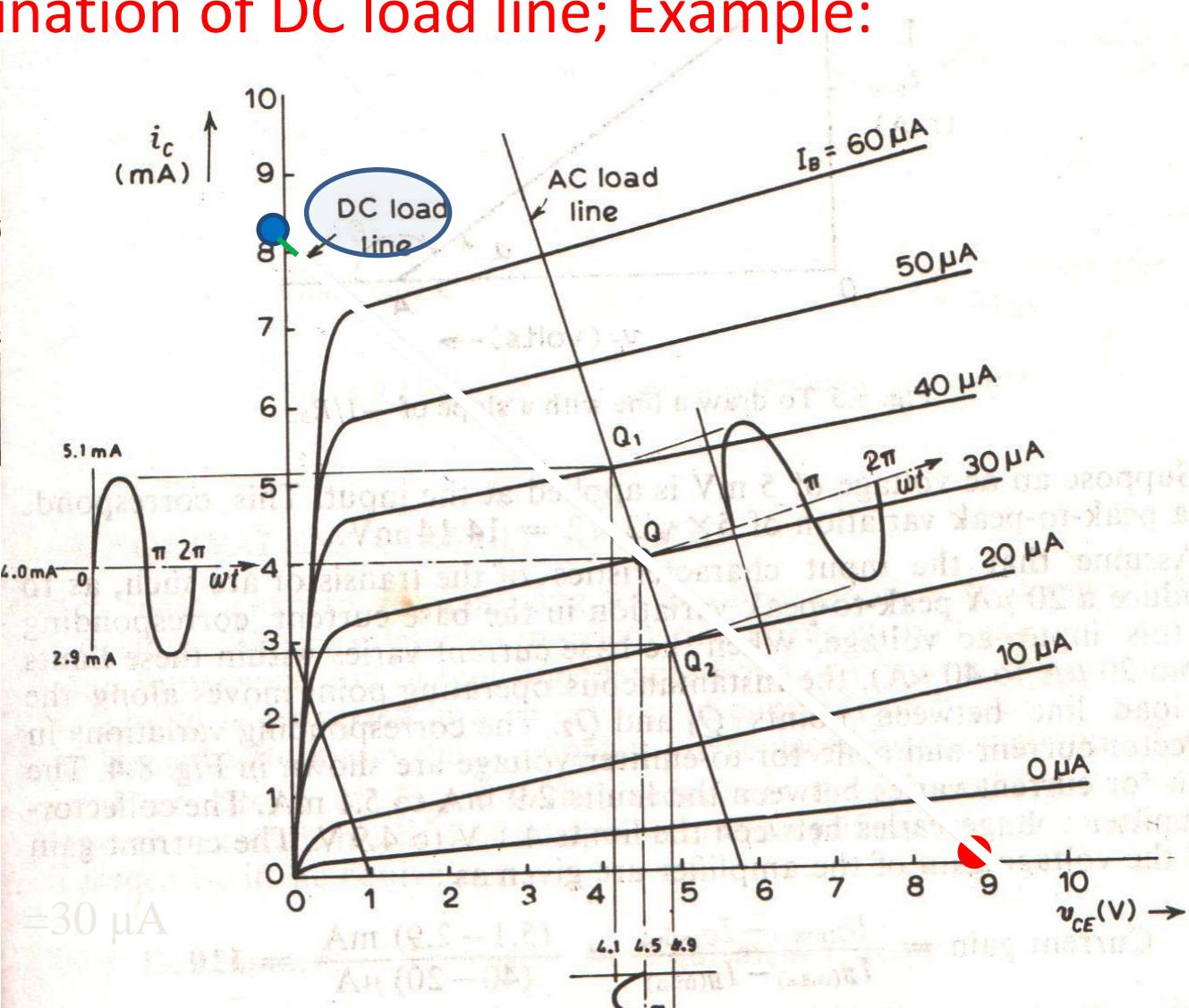

# Graphical Method: DC Analysis
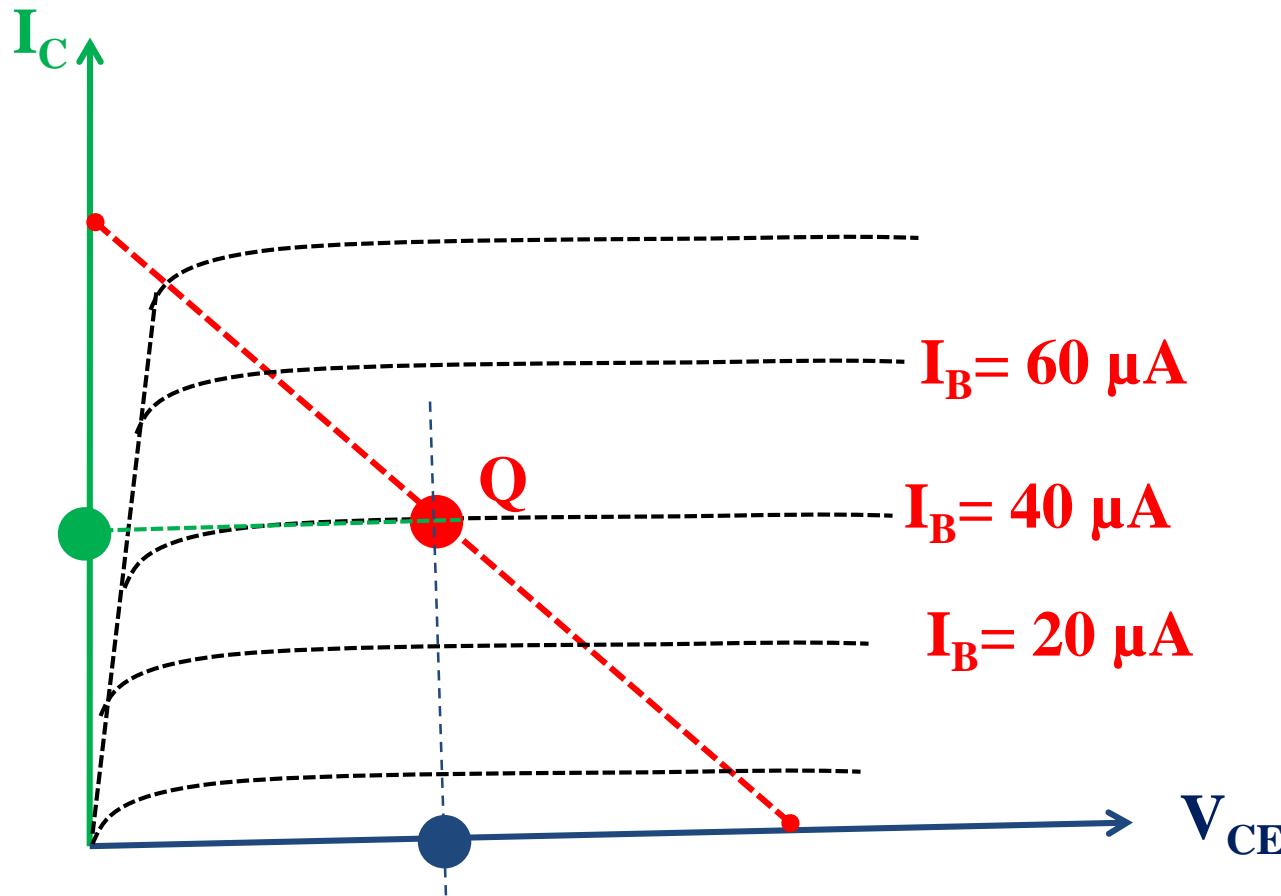
## DC Load line Variations in Q with DC bias ( $I_B$ )



But with AC signal, changes in  $Q$  are very fast.


# Graphical Method: AC Analysis

We need two Considerations:

1. The capacitive reactance is  $X_c = 1/(2\pi fC)$   $\Omega$ . It indicates that the coupling & emitter by-pass capacitor can be approximated as **short circuit** at high enough frequency.
2. Since, we deal with only ac voltages we do need **not to consider effect of dc voltages/currents** in the circuit.


With these two considerations the amplifier circuit can be modeled for equivalent circuit.

# Graphical Method: AC Analysis

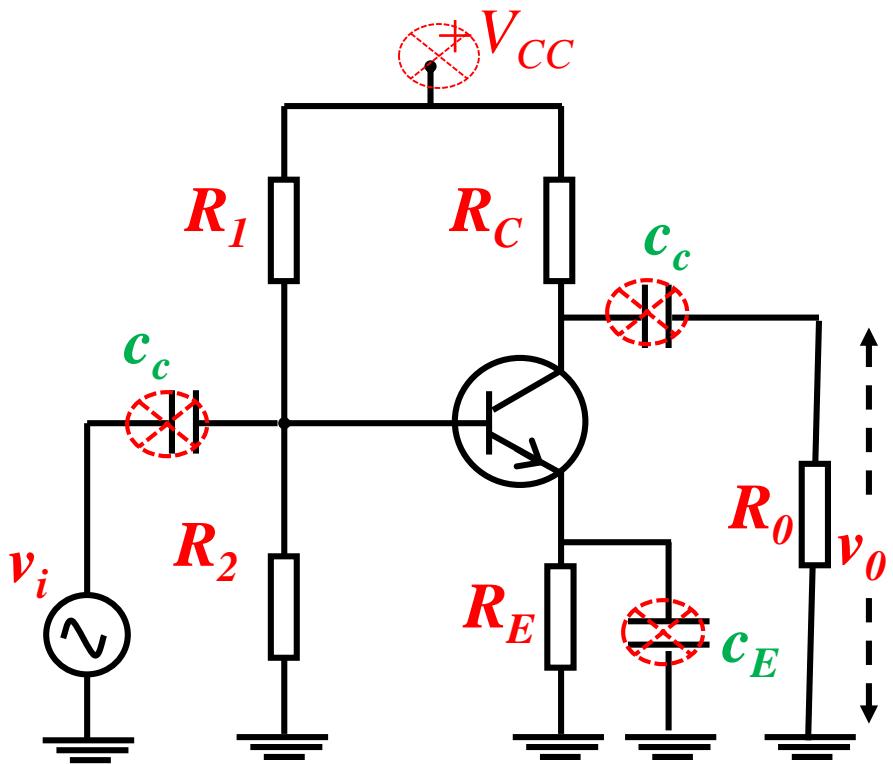

Basic CE Circuit

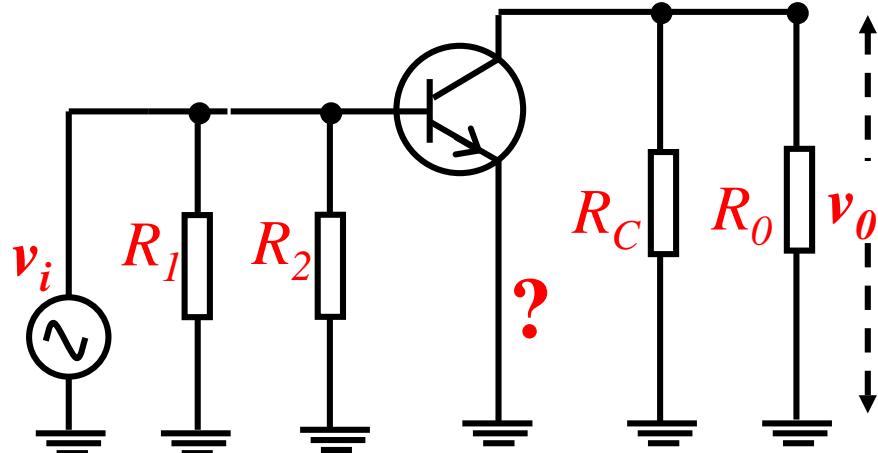1. Effect of  $C_c$ 's and  $C_E$
2. DC supply Shorted




AC behavior

Where is  $R_E$ ?

# Graphical Method: AC Analysis

AC behavior:

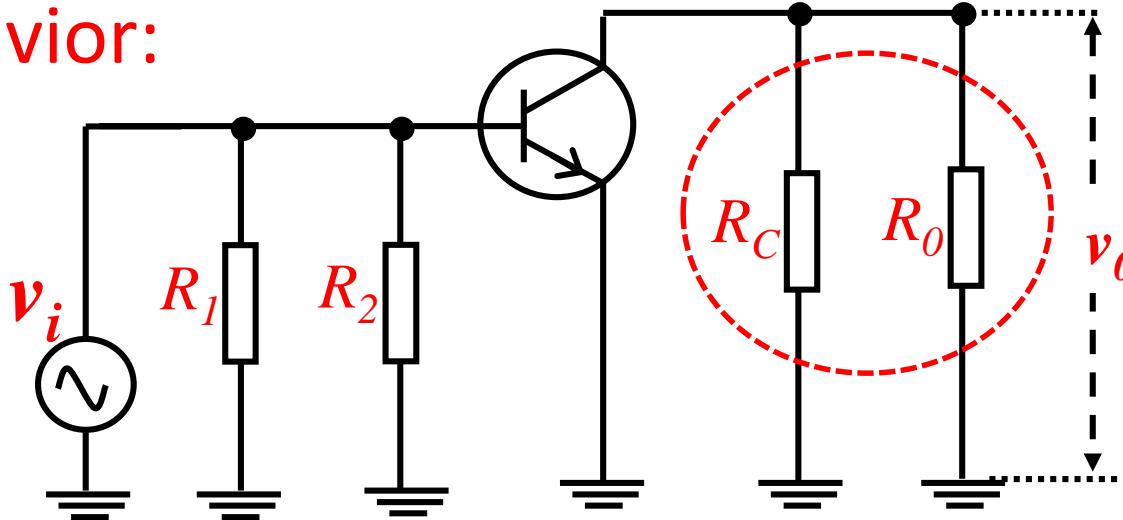


As shown,  $R_C$  and  $R_O$  in parallel forms the ac load  $R_{ac}$ .

The load line corresponding to this  $R_{ac}$  is ac load line


Since  $R_{dc}$  and  $R_{ac}$  are different, DC and AC load lines are different. However both must pass through Q point for zero signal condition.
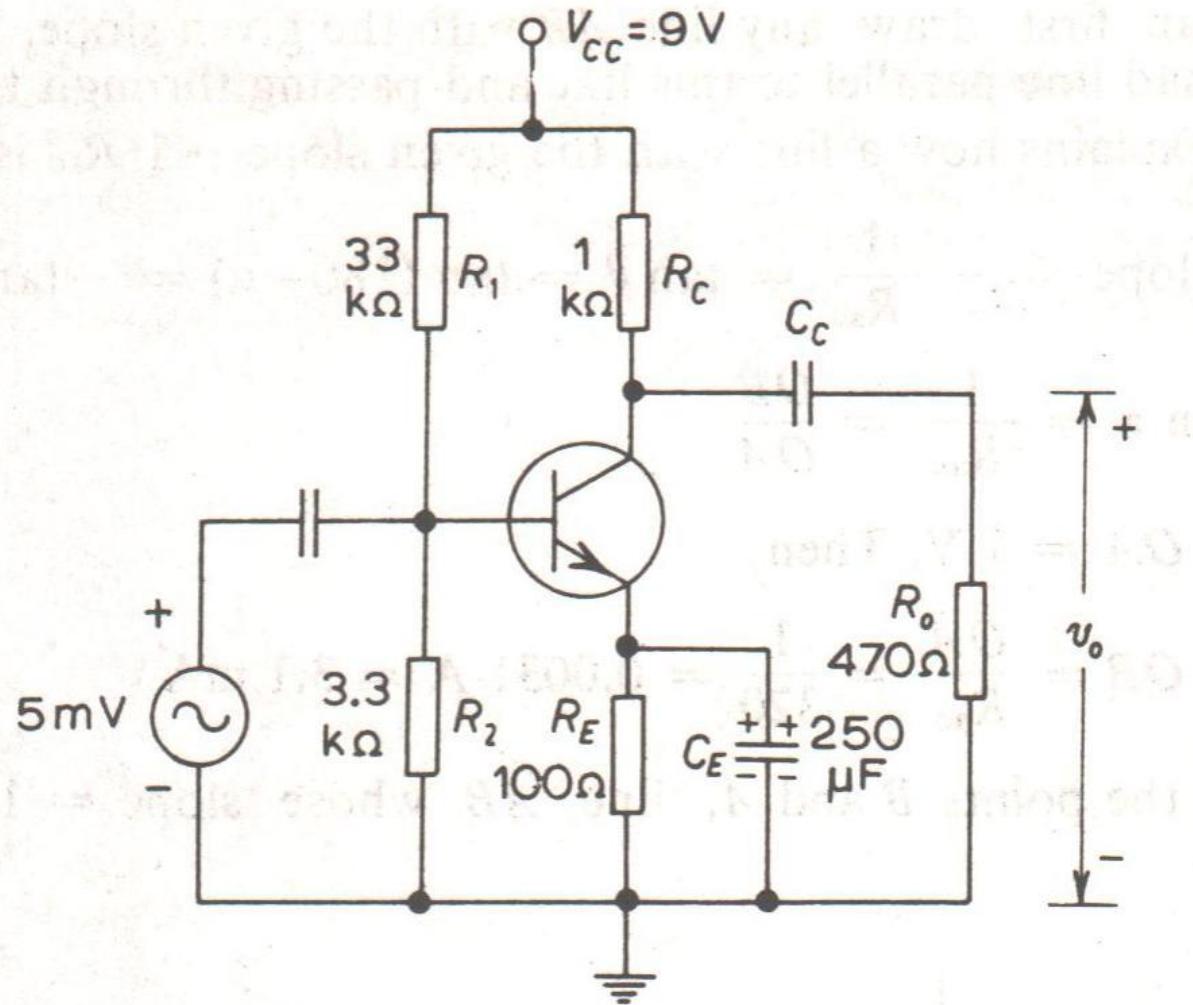
# Graphical Method: AC Analysis

Determine the AC load line of the circuit.


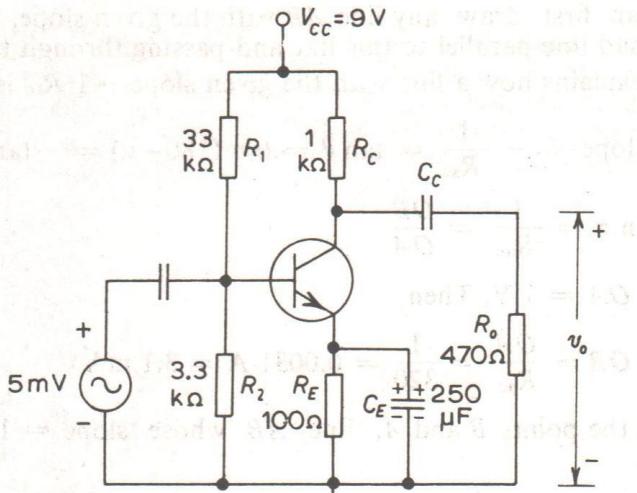
# Graphical Method: AC load line; Example



With AC signal

$$R_{ac} = R_C \parallel R_o = 320 \Omega$$

$$\text{and so } 1/R_{ac} = 0.0031$$

Slope of ac load line =  $1/R_{ac}$


Draw line AB with

slope =  $OB/OA = 1/R_{ac}$


If we set  $OA = 1V$  then slope =  $1/R_{ac} = OB/1V$ .

So we get  $OB = (1V/R_{ac})$  Ampere = 3.1 mA.


Hence we get co-ordinates of point B.

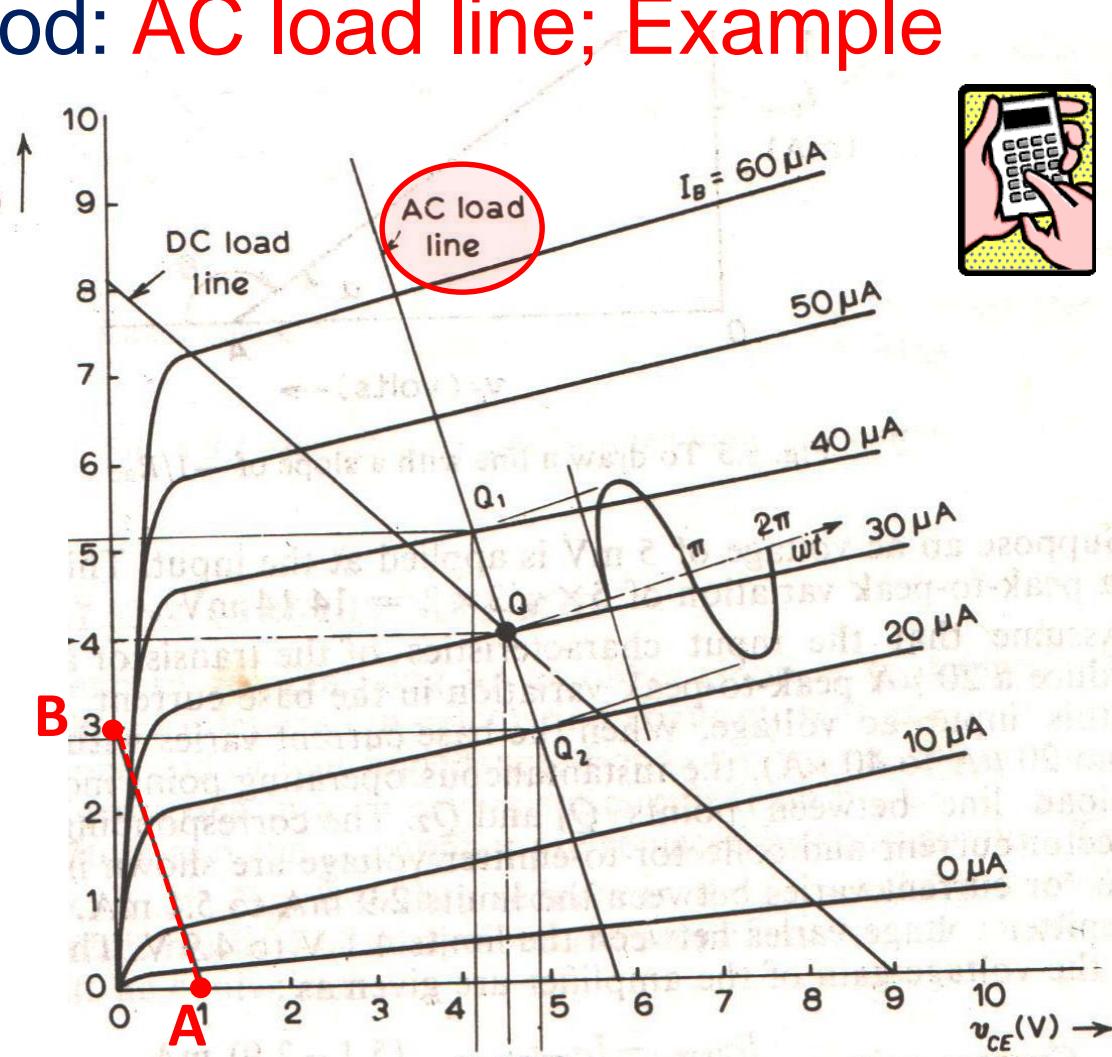

# Graphical Method: Calculation of Gain

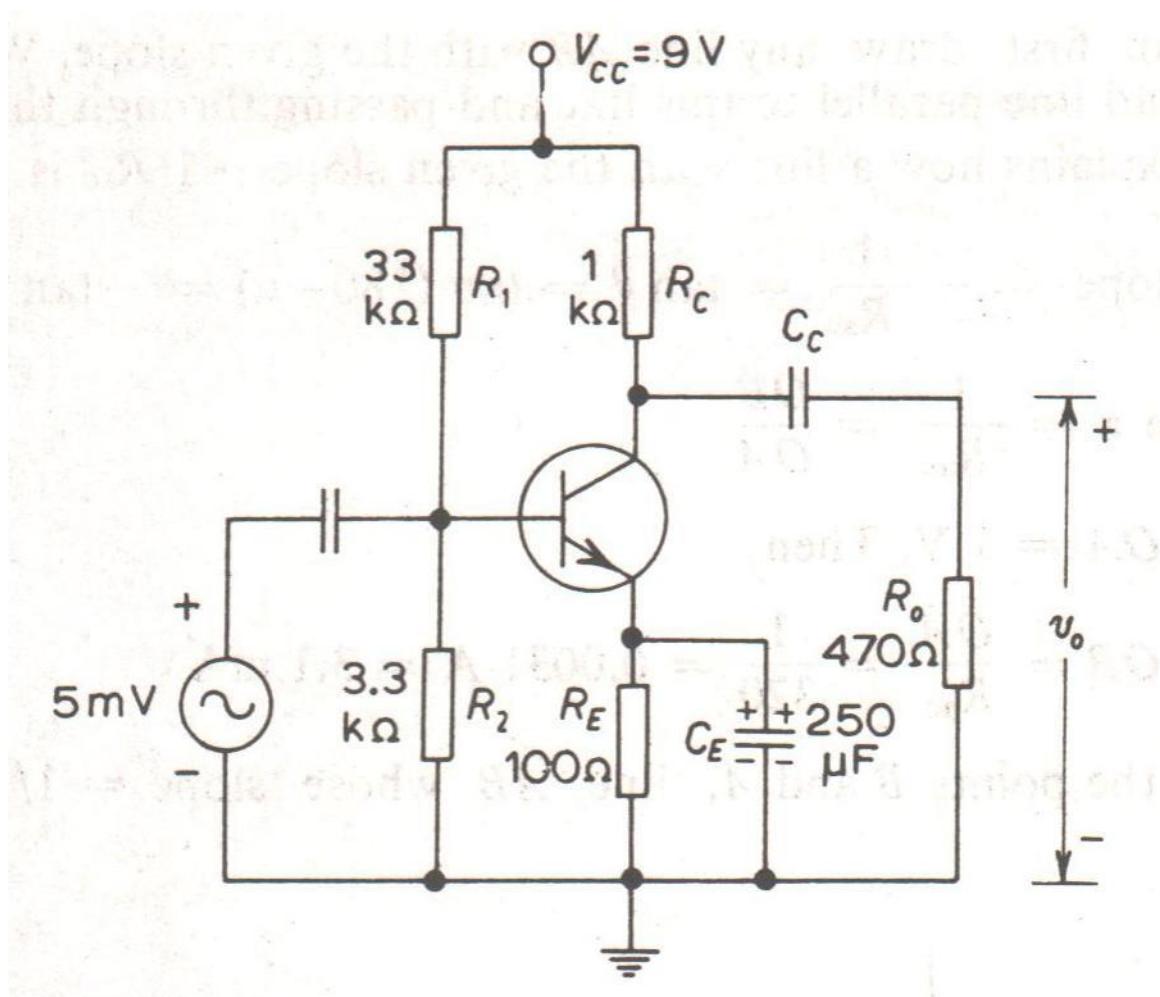

# Graphical Method: Calculation of Gain

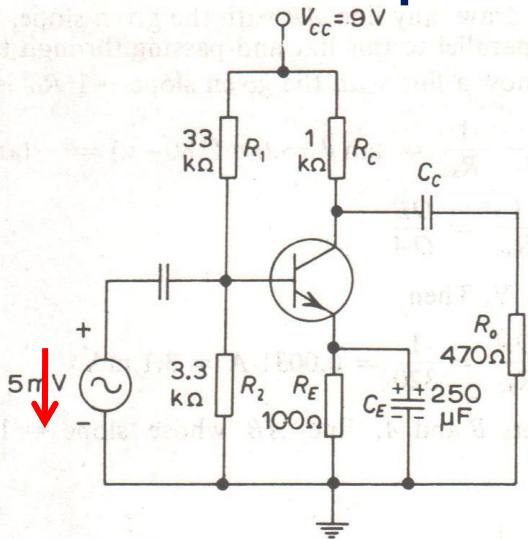


With AC signal of 5 mV,  
peak to peak variation  
are  $5 \times 2 \times \sqrt{2} = 14.14 \text{ mV}$

Voltage Gain


$$\begin{aligned} A_v &= (V_{CE \max} - V_{CE \min}) / (V_i \max - V_i \min) \\ &= (4.9 - 4.1) \text{ V} / (14.14) \text{ mV} \\ &= 56.58 \end{aligned}$$

Current Gain

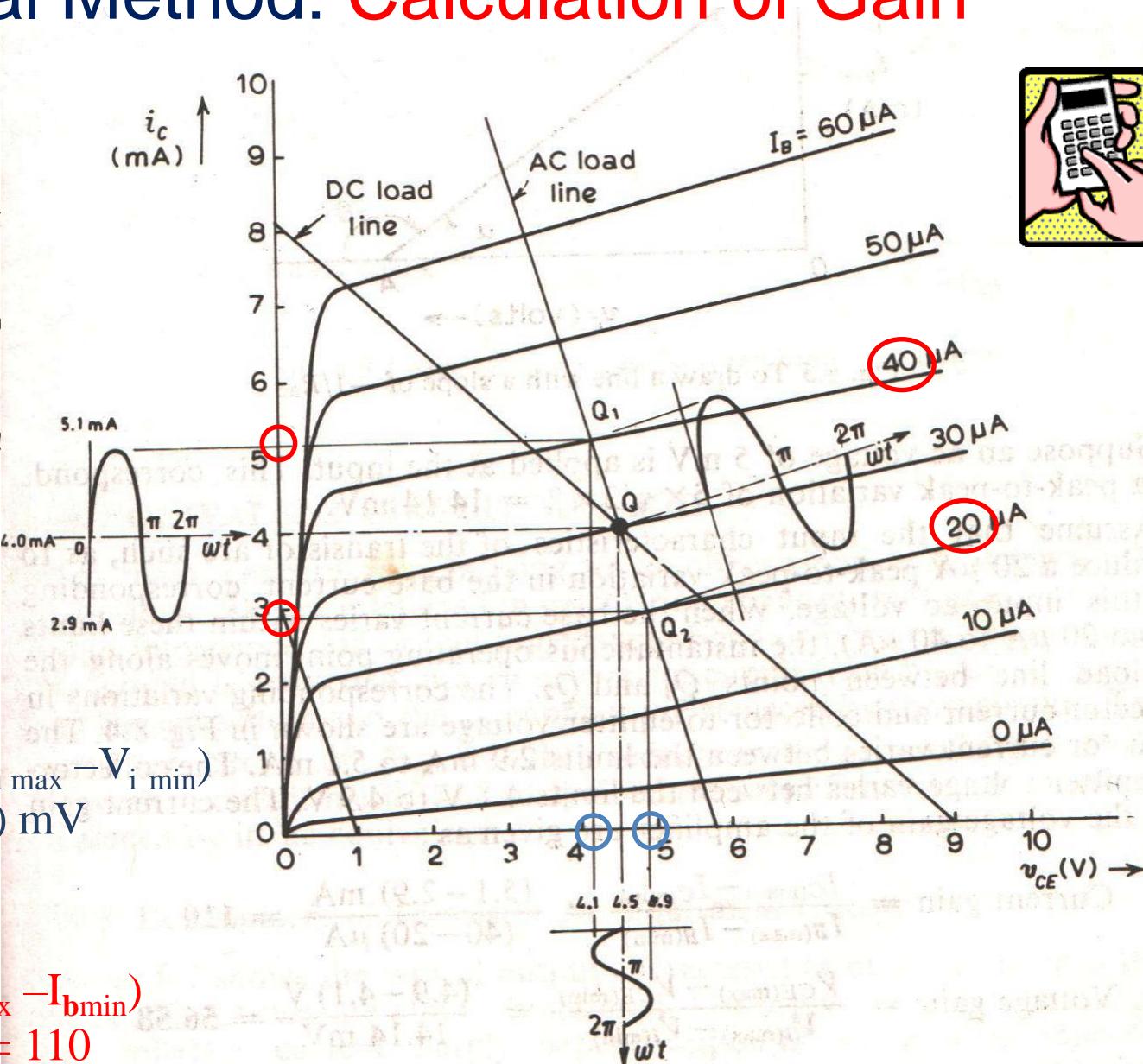
$$\begin{aligned} &= (I_C \max - I_C \min) / (I_B \max - I_B \min) \\ &= (5.1 - 2.9) / (40 - 20) = 110 \end{aligned}$$



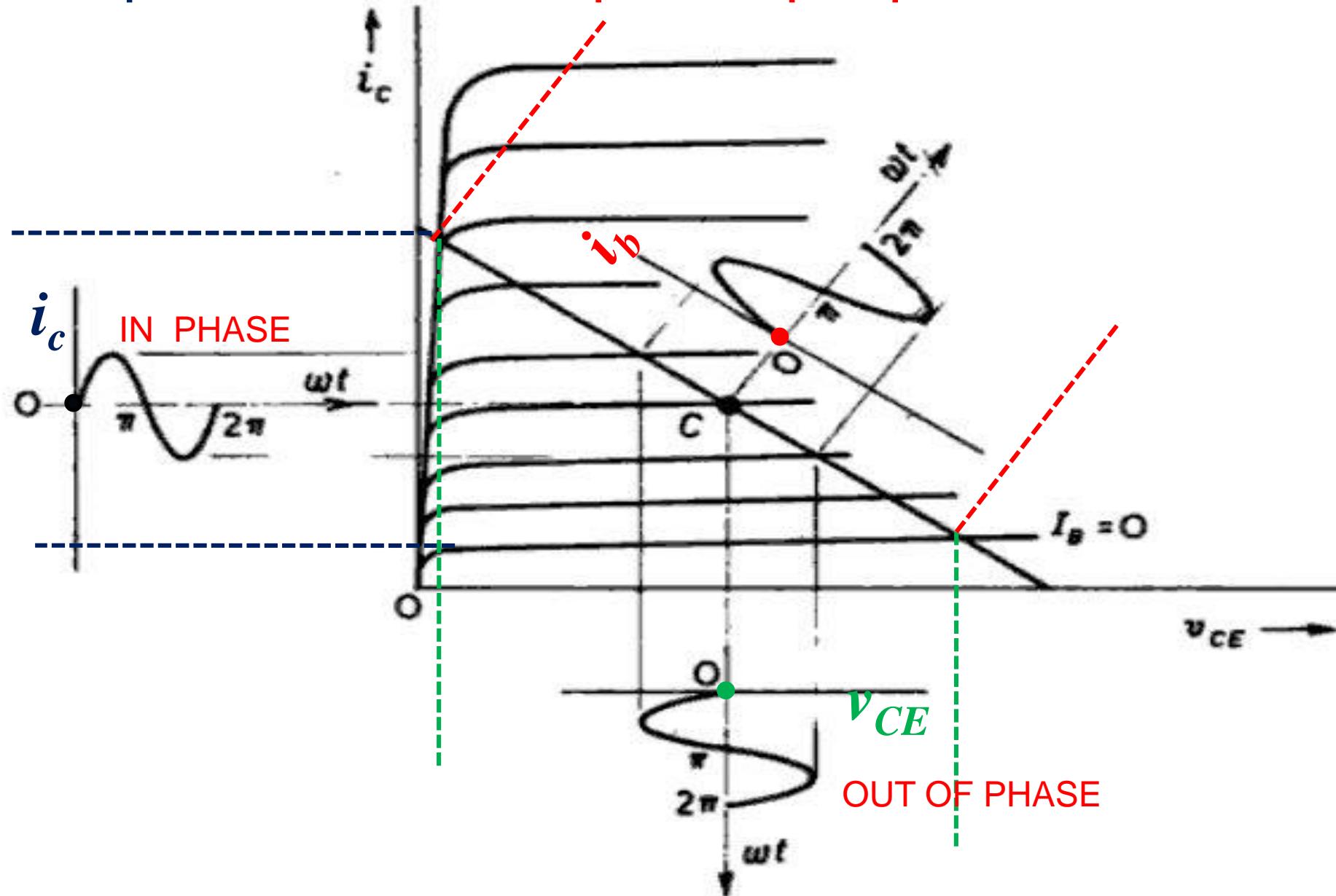
# Graphical Method: input-output phase relations



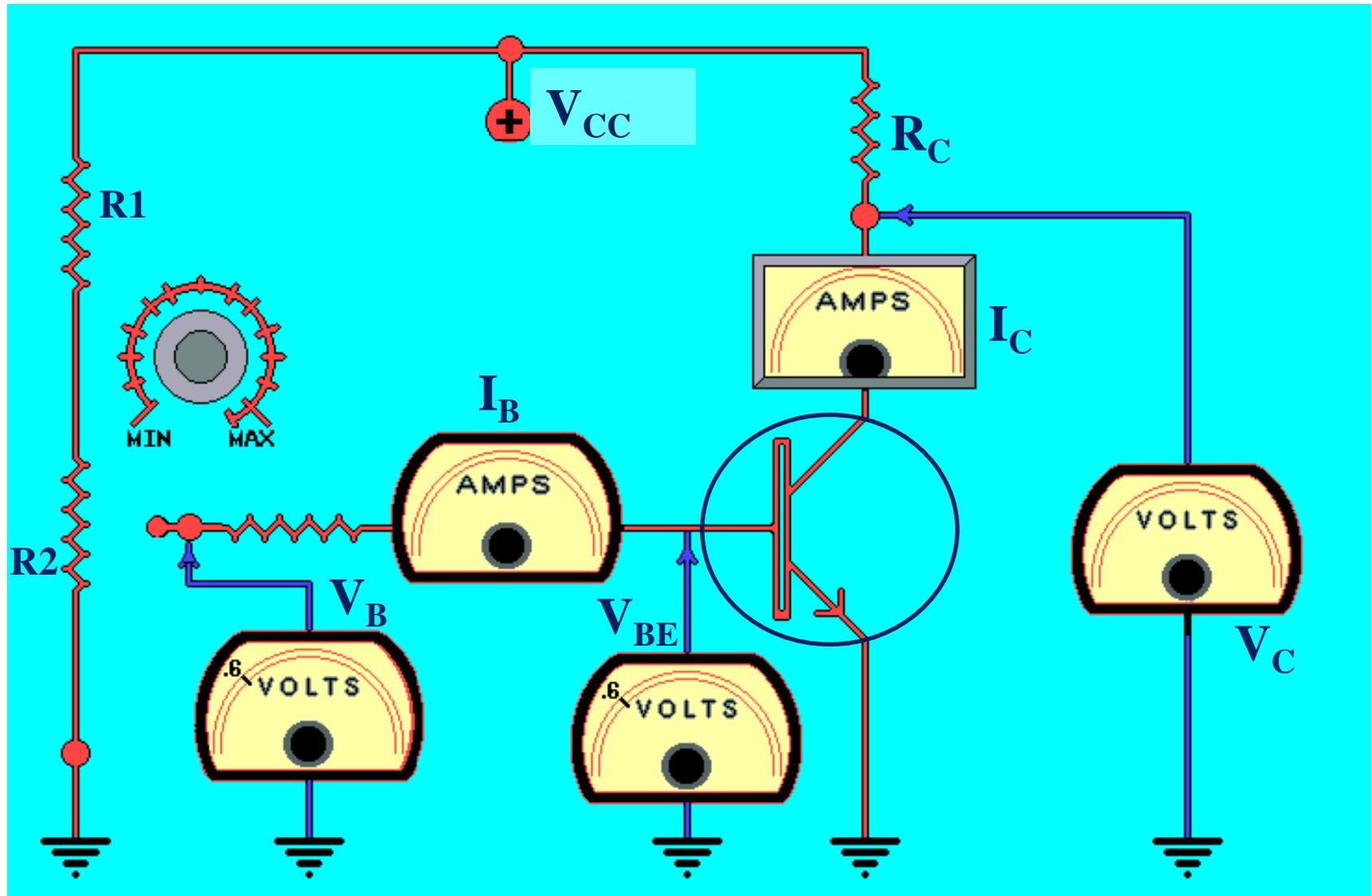
# Graphical Method: input output phase relations



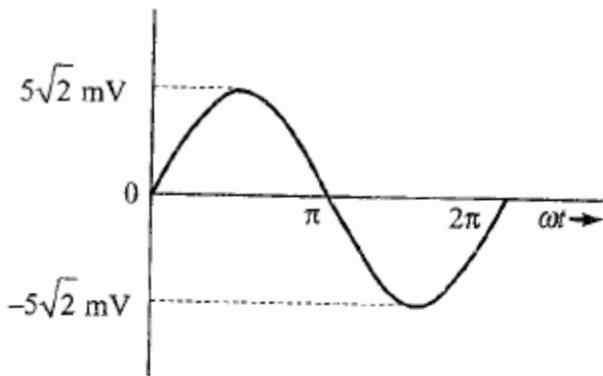
# Graphical Method: input output phase relations




(a) Input voltage

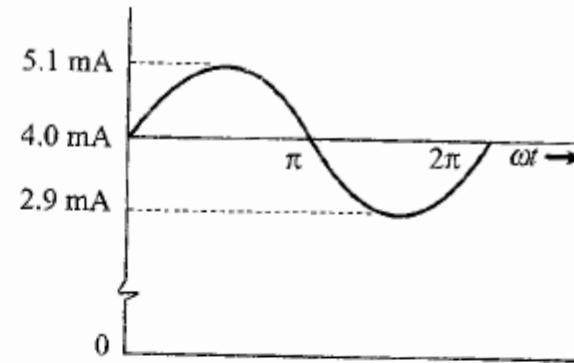

(c) Collector current

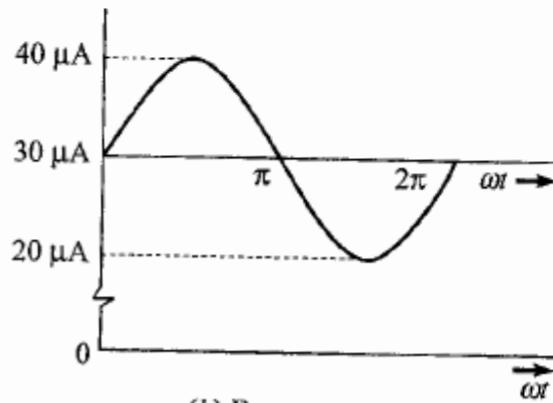

(b) Base current

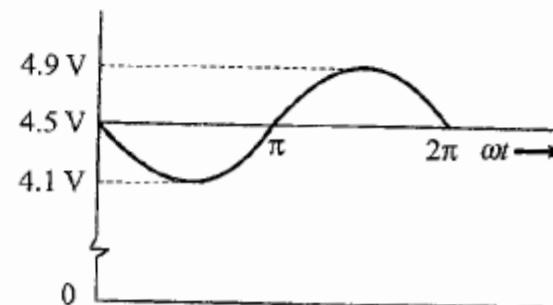

(d) Collector-to-emitter (output) voltage

Reference Book:  
Basic Electronics and Linear Circuits  
N N Bhargava  
D C Kulshreshtha  
S C Gupta