

[33]

**SARDAR PATEL UNIVERSITY**  
**BSC (6<sup>th</sup> SEMESTER EXAMINATION)**  
**ELECTRONICS**  
**US06CELE22**  
**Digital Systems**

Date: 16/07/2021

Time: 10:00 A.M. To 12:00 P.M.


Day: Friday

Total marks: - 70

Q:1 Multiple Choice Questions.

[10]

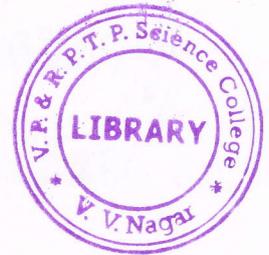
- (1) In tri – state switch the output is low, high or \_\_\_\_\_.  
(a) Floating            (b) two            (c) three
- (2) Fusible links are used in \_\_\_\_\_ type of memory.  
(a) PROMs            (b) ROMs            (c) EPROMs
- (3) CCD is type of \_\_\_\_\_ memory.  
(a) Dynamic            (b) Static            (c) Both (a) & (b)
- (4) The full form of PAL \_\_\_\_\_.  
(a) Programmable Array Logic  
(b) Programmable And Logic  
(c) Programmable Logic device
- (5) D to A is a part of \_\_\_\_\_ converter.  
(a) D/A            (b) A/D            (c) D/D
- (6) Magnetic core memory is a \_\_\_\_\_ memory.  
(a) Volatile            (b) Non Volatile            (c) None of above
- (7) Flash type ADC is a \_\_\_\_\_ Converter.  
(a) Fastest            (b) Slowest            (c) Medium
- (8) Op- amp is used as a \_\_\_\_\_ in successive approximation.  
(a) Inverting amplifier            (b) Comparator            (c) Non – inverting amplifier.
- (9) Successive approximation converter is \_\_\_\_\_ A/D converter.  
(a) Slowest            (b) Medium            (c) Fastest
- (10) The full form of EPLD is \_\_\_\_\_.  
(a) Erasable programmable logic device  
(b) Erasable programming level device  
(c) Electrically programmable logic device



Q:2 State whether the following statements are true or false. [08]

- (1) The static RAM can store data as long as power is applied to the chip.  
True/false
- (2) A storage element is called cell. True/false
- (3) An IC ADC 0801 has eight bit output. True/False
- (4) Semiconductor memories are faster than magnetic memory. True/False.
- (5) PLD is also called Programmable logic sequencer. True/False.
- (6)  $2^n - 1$  comparators are required to construct n-bit flash type A/D converter. True/False
- (7) A counter type A/D converter uses up – down counter. True/False
- (8) In V/F type A/D convertor time is constant. True/ False.

Q:3 Answer any ten questions in brief :

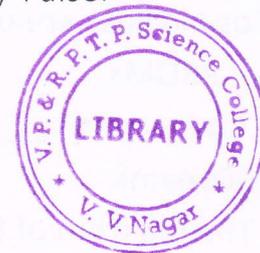

[20]

- (1) Give an account of ECL RAM
- (2) State the difference between static RAM and dynamic RAM.
- (3) Give introduction of FPLA.
- (4) Draw the basic structure of PAL circuit.
- (5) List the parameters of DAC.
- (6) What are the advantage and disadvantage of Flash type A/D converter?
- (7) Draw the block diagram of successive approximation A/D converter.
- (8) List of specification of A/D converter.
- (9) Draw the figure of dynamic memory cell and explain it in brief.
- (10) Calculate the number of resistor and comparators required in 3 – bit flash type A/D converter.
- (11) Draw the circuit diagram of weighted resistor type DAC.
- (12) What do you mean by A/D conversion?

Q:4 Long answer questions ( Attempt any four out of eight) [32]

- (i) Explain semiconductor RAMs. [08]

(2)

[P.T.O]

- (ii) Explain type of ROM in detail. [08]
- (iii) Explain various programmable logic devices in detail. [08]
- (iv) Explain 4 bit R-2R ladder type DAC in detail. [08]
- (v) Explain magnetic memory in detail. [08]
- (vi) Explain voltage to frequency type A/D converter with necessary diagrams. [08]
- (vii) Explain Counter type A/D converter. [08]
- (viii) Explain voltage to Time A/D converter with necessary diagrams. [08]

— x —

(3)

