

V.P. & R.P.T.P. SCIENCE COLLEGE  
VALLABH VIDYANAGAR



First Semester B.Sc. Internal Examination

Subject: Physics Title: Network Analysis, Optics and Laser Course: USO1CPHY02

Date: 05 -12-2014 Friday Time: 11:00 to 12.00 pm

Total Marks:25

- Q.1 Answer the following questions with the correct choice. (Each of 1 Mark.) (3)**
- (1) The point of a network where three or more circuit elements are connected is known as ..... point.  
(a) junction (b) node (c) branch (d) mesh.
  - (2) Which of these is not a dc bridge?  
(a) Kelvin bridge (b) Maxwell bridge (c) Wheatstone bridge (d) none of these
  - (3) For a transmission grating, with decrease in spectrum order (n), the resolving power  
(a) increases (b) decreases (c) becomes infinite (d) remains unchanged
- Q.2 Answer any two. (Each of 2 Mark.) (4)**
- (1) Give statement of Thevenin's theorem and state its importance.
  - (2) Draw the circuit of dc bridge and state expressions for its balancing conditions.
  - (3) Define resolving power and state Rayleigh's criterion for just resolved images.
- Q.3 With a suitable diagram explain what is a network and define various network terms i.e. network terminology. (6)**
- OR**
- Q.3 Define mesh and mesh current. Explain mesh current method for analysis of a two mesh network with a proper example. (6)**
- Q.4 With necessary diagram explain construction and working of Maxwell bridge. Mention its limitations. (6)**
- OR**
- Q.4 What is a Wien Bridge? With necessary diagram explain its working and discuss its parameters. (6)**
- Q.5 What is an interferometer? Explain principle, construction and working of a Michelson interferometer. (6)**
- OR**
- Q.5 Explain resolving power of a microscope and derive expression for it. (6)**