

First Semester B.Sc. Internal Examination

Subject: **Physics**


Course: **USO1CPHY02**

Date: **07 -10-2015 , Wednesday Time: 1:30 to 2:30 pm**

Total Marks:**25**

Q.1 Answer the following questions with the correct choice. (Each of 1 Mark.) (3)

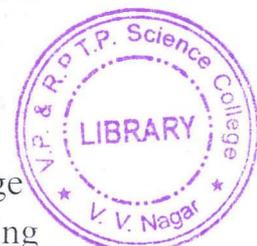- (1) The point of a network where three or more circuit elements are connected is known as point.
(a) junction (b) node (c) branch (d) mesh.
- (2) Which of these bridges is used to determine capacitance of a capacitor?
(a) Kelvin bridge (b) Schering bridge (c) Hay bridge (d) Maxwell bridge
- (3) For a transmission grating, with increase in spectrum order (n), the resolving power
(a) becomes infinite (b) decreases (c) increases (d) remains unchanged



Q.2 Answer any TWO. (Each of 2 Mark.) (4)

- (1) State Superposition principle and explain its importance.
- (2) Draw the circuit of ac bridge and state expressions for its balancing conditions.
- (3) There are total 40,000 lines (i.e. N) ruled on a plane transmission grating. Determine its resolving power in the second order (i.e. n=2).

Q.3 With a suitable diagram explain what is a network and define various network terms i.e. network terminology. (6)

OR

Q.3 With a suitable diagram explain mesh and mesh current. Explain mesh current method for analysis of a three mesh network. (6)

Q.4 With necessary diagram explain construction and working of Hay bridge. Mention its importance. (6)

OR

Q.4 What is a Wein Bridge? With necessary diagram explain its working and discuss its parameters. (6)

Q.5 State principle of Michelson interferometer. Explain construction and working of a Michelson interferometer. (6)

OR

Q.5 Define resolving power of a prism and derive expression for it. (6)