

Extra

V.P. & R.P.T.P SCIENCE COLLEGE
INTERANAL EXAM
S.Y.B.Sc.(SEM-III) INSTRUMENTATION (VOC.)

SUB: - Operational amplifiers and filters

Sub. Code: US03CINV23

DATE:-03/10/2019

TIME: 3:00 pm to 4:15 pm

MARKS-25

- Q-1 Choose correct answer [05]
- When the two terminals are to be at same potential hence two input terminal are said to be _____.
(A) virtually grounded (C) virtually shorted
(B) actually grounded (D) None of above
 - _____ gives the triangular output when input is square wave.
(A) Adding integrator (C) Differentiator
(B) Comparator (D) integrator
 - _____ multivibrator is also called free running oscillator.
(A) Astable (C) Critical
(B) Monostable (D) None of above
 - Active filter use _____ components basically for filtration.
(A) copper loss (C) iron core
(B) ferrite loss (D) None of above
 - In band pass filter _____ frequency is eliminated.
(A) low and high (C) intermediate
(B) high (D) low
- Q-2 Explain the block diagram of op-amp. [05]
OR
- Q-2 Derive the expression for inverting amplifier with feedback. [05]
- Q-3 Draw the circuit of differential op-amp and derive an equation [05]
 $V_{out} = -R_f/R_1(V_X - V_Y)$.
OR
- Q-3 Explain basic comparator and draw the waveforms using op-amp. [05]
- Q-4 Draw the circuit diagram of pulse-width modulation(PWM) and [05]
Explain it with necessary waveform.
OR
- Q-4 Explain the Monostable multivibrator. [05]
- Q-5 Explain data acquisition circuit using instrumentation operational amplifier. [05]
OR
- Q-5 Give an account of active low pass first order butter worth filter. [05]

