

V. P. & R. P. T. P. Science College  
FIRST UNIT TEST  
US05CELE04

4/10/2016  
11:00 am to 12:30 pm  
25 marks

**Multiple Choice Questions: (Any 3)**

3 marks

1. At the null condition the current through the detector is
  - (i) minimum.
  - (ii) maximum.
  - (iii) zero.
2. Schering bridge is used to measure capacitance of a capacitor whose phase angle is
  - (i) is nearer to  $90^\circ$ .
  - (ii) is lower than  $90^\circ$ .
  - (iii) is equal to  $90^\circ$ .
3. Transducer forms a part of \_\_\_\_\_ in instrumentation system.
  - (i) Input device
  - (ii) Output device
  - (iii) Processing device



**Q. 2 Short Questions: (Any 2)**

4 marks

1. State two differences between ac and dc bridge.
2. What do you mean by Dissipation factor. What does it tell?
3. Define Transducer.

**Q.3 Describe in detail Kelvin double bridge.**

6 marks

**OR**

**Q.3** The ac bridge is in balance with following constants. Arm AB,  $R=450 \Omega$ , Arm BC,  $R=300 \Omega$  in series with capacitor  $C=0.256 \mu\text{F}$  and arm CD unknown, arm DA,  $R=200 \Omega$  in series with inductor  $L=15.9 \text{ mH}$ . The oscillator frequency is 1 KHz. Find the constants of arm CD.

6 marks

**Q.4 Describe in detail Schering bridge and show that the dial of Schering bridge can be calibrated directly in terms of dissipation factor D.**

**OR**

**Q.4 Describe in detail working of Wein bridge.**

6 marks

**Q.5 Write short note on Transduce.**

6 marks

**OR**

**Q.5 Describe in detail LVDT.**

6 marks

\*\*\*\*\*BEST OF LUCK\*\*\*\*\*