

Extra

V. P. & R. P. T. P. SCIENCE COLLEGE

Vallabh Vidyanagar

Internal Test

BSc [Semester - V] Subject: Physics Course: US05CPHY05

Title: Analog Devices and Circuits

Date: 05-10-2016, Wednesday

Time: 11 am to 12.30 pm

Total Marks 25



Q-1 Multiple Choice Questions: [One mark each] 3

- [i] Transconductance is measured in _____.
(a) Ohm (b) Mho (c) Siemen (d) both (b) and (c)
- [ii] The correct relationship is _____.
(a) $f_{\beta} < f_T < f_{\alpha}$ (b) $f_{\beta} < f_{\alpha} < f_T$ (c) $f_{\alpha} < f_{\beta} < f_T$ (d) $f_{\beta} = f_T = f_{\alpha}$
- [iii] The number of biasing resistor(s) used in a pure class B push pull amplifier is/are _____.
(a) One (b) Two (c) Three (d) Zero

Q-2 Answer any two questions in short. [Two marks each] 4

- [A] The JFET has $I_{DSS} = 10 \text{ mA}$ and $V_P = 2 \text{ V}$, then $R_{DS} = \text{_____} \Omega$.
- [B] List four h-parameters of CE transistor amplifier.
- [C] If $D_2 = 4\%$, $D_3 = 0\%$, $D_4 = 3\%$ and $D_5 = 9\%$, calculate total harmonic distortion (D_T) of the power amplifier.

Q-3 Discuss any two biasing circuits of JFET amplifier. 6

OR

Q-3 Discuss any two applications of JFET. 6

Q-4 Discuss hybrid π -model to study the high frequency response of CE amplifier. 6

OR

Q-4 Discuss effect of coupling capacitor and bypass capacitor on low-frequency response of the CE transistor amplifier. 6

Q-5 Explain design theory for power amplifier. 6

OR

Q-5 Define conversion efficiency of an amplifier. Prove that conversion efficiency of class B push pull amplifier is equal to 78.5%. 6

=====