

Extra

V.P & R.P.T.P SCIENCE COLLEGE
First Internal Test
US05CELE-04

Date: 6/10/17
11:30 to 5:00 pm
Total Marks 30



Q-1 Multiple choice questions:

3 marks

- (1) The Maxwell bridge is used to measure
- (i) low value resistors
 - (ii) Capacitor
 - (iii) Inductor
 - (iv) High value resistors
- (2) Power factor is defined as
- (i) cosine of phase angle.
 - (ii) cotangent of phase angle.
 - (iii) sine of phase angle.
 - (iv) Tangent of phase angle
- (3) Transducer forms a part of _____ in instrumentation system.
- (i) Input device
 - (ii) Output device
 - (iii) Processing device
 - (iv) None of the above

Q2: Answer in short: (any 2)

4 marks

1. State two conditions to be satisfied simultaneously to balance an ac bridge.
2. What do you mean by Dissipation factor. What does it tell?
3. Define Transducer and classify them.

6 marks

Q-3 Derive an expression for unknown resistance using Kelvin Double Bridge.

OR

Q-3a Give two differences between ac and dc bridges.

2marks

Q-3b The ac bridge is in balance with following constants, arm AB, $R=450 \Omega$, arm BC $R=300 \Omega$ in series with capacitor $C = 0.256$ micro Farad, arm CD unknown, arm DA

$R = 200 \Omega$ in series with inductor $L = 15.9 \text{ mH}$. The oscillator frequency is 1 kHz . Find the constants of arm CD. **4 marks**

Q-4 Describe in detail Schering bridge and show that the dial of Schering bridge can be calibrated directly in terms of dissipation factor D . **6 marks**

OR

Q-4 Describe in detail Hay bridge and show that it is suitable for the measurement of High Q coil. **6marks**

Q-5 Write shortnote on Transducers. **6marks**

OR

Q-5 Discuss in detail working of LVDT. **6 marks**

*****Best of Luck*****

