



VP & RPTP SCIENCE COLLEGE
Vallabh Vidyanagar
First Internal Test

BSc [Semester - V] Subject: Physics Course: US05CPHY05
Title: Analog Devices and Circuits


Date: 6-10-2018, Saturday
Total Marks 50

Time: 10 am to 12 noon

Q-1 Multiple Choice Questions: [One mark each]

8

[1]

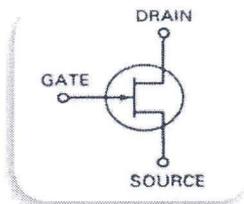

is a symbol of _____

- (a) n- channel FET (b) p-channel FET
(c) E-MOSFET (d) D-MOSFET

[2] _____ is used to bias the FET in ohmic region.

- (a) Voltage-divider bias (b) Self-bias (c) Gate bias (d) Source bias

[3] The lower cut off frequency of CE transistor amplifier is independent only upon:

- (a) C_e (b) C_c (c) R_s (d) R_e

[4] If $h_{fe} = 100$, $h_{fb} = 0.97$, $f_{\alpha} = 330$ MHz and $f_{\beta} = 300$ MHz, the gain bandwidth product (f_T) in CB configuration is equal to _____.

- (a) 320.1 MHz (b) 291 MHz (c) 30000 MHz (d) 33000 MHz

[5] Conversion efficiency of a class-A CE power amplifier with direct coupled resistive load is _____.

- (a) 25 % (b) 50 % (c) 78.5 % (d) 100 %

[6] The harmonic distortion is due to _____ nature of the _____ devices.

- (a) linear, active (b) nonlinear, active
(c) nonlinear, passive (d) linear, passive


[7] If $R_f = 10$ K Ω and $R = 2$ K Ω , the voltage gain of an ideal inverting mode OpAmp is equal to _____.

- (a) 20 (b) -20 (c) 5 (d) -5

[8] In which application of OpAmp, a diode is connected as feedback element with input element is resistor?

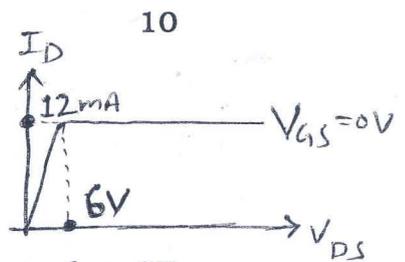- (a) Summing amplifier (b) Difference amplifier
(c) Logarithmic amplifier (d) Weighted amplifier

Q-2 Answer the following questions in short.
(Attempt any FIVE questions) [Two marks each]:



- [1] Write any four advantages of FET compared to BJT.
- [2] In a given drain characteristic of JFET, $I_{DSS} = \underline{\hspace{1cm}}$, $V_P = \underline{\hspace{1cm}}$, ohmic resistance $R_{DS} = \underline{\hspace{1cm}}$ and the gate-source cutoff voltage $V_{GS(off)} = \underline{\hspace{1cm}}$.
- [3] What are the factors on which high frequency response of a CE amplifier depends? Explain it with necessary equations.
- [4] Discuss classification of small signal tuned amplifiers.
- [5] Define conversion efficiency of an amplifier.
- [6] Draw labeled circuit diagram of other class B push pull amplifier without transformer.
- [7] What are the characteristics of an ideal operational amplifier?
- [8] List Op-Amp parameters and define any two.

Q-3 (a) Draw and describe transconductance curves of FET. 5
A2N5459 has $V_{GS(off)} = -8\text{ V}$ and $I_{DSS} = 16\text{ mA}$. What is the drain current at the half cutoff point?

Q-3 (b) Write a note on MOSFET. 3

OR

Q-3 (a) List any FIVE applications of JFET and describe any two. 5

Q-3 (b) List name of the biasing circuits which bias JFET in the active region and describe any one. 3

Q-4 Define and explain h-parameters of the transistor. 8

OR

Q-4 Derive the following amplifier equations: 8
(1) Current gain (2) Input resistance and (3) Voltage gain.

Q-5 (a) Describe an operation of class A push pull amplifier. 5

Q-5 (b) Explain how class A push pull amplifier removes all even harmonics? 3

OR

Q-5 (a) Write a note on class B push pull amplifier. 5

Q-5 (b) Draw circuit diagram of transistor phase inverter and describe working of it. 3

Q-6 (a) Draw a circuit diagram of differential amplifier having dual input balanced output configuration. Derive expressions for Q-point of the circuit. 5

Q-6 (b) Describe use of Op-Amp as integrator. 3

OR

Q-6 (a) Write a note on the noninverting summing amplifier using Op-Amp. Derive an expression for its voltage gain 5

Q-6 (b) Calculate the output voltage of an OpAmp inverting adder for the following sets of input voltages and resistors. In all cases $R_f = 1000\text{ K}\Omega$, $V_1 = -3\text{ V}$, $V_2 = 1\text{ V}$, $R_1 = R_2 = 500\text{ K}\Omega$. 3

