

V.P. & R.P.T.P SCIENCE COLLEGE

INTERANAL EXAM

T.Y.B.Sc.(SEM-V) ELECTRONICS

SUB: - Digital systems

SUB CODE: US05CELE02


DATE: 03/10/2019

TIME: 11:00 pm to 12:15 pm

MARKS-25

Q-1 Choose correct answer [05]

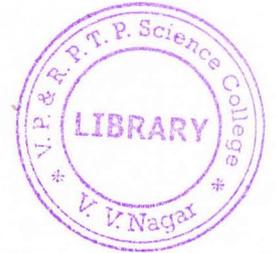1. Registers are made of _____.
(A) flip-flops (C) Resistor
(B) capacitor (D) None of above
2. In controlled buffer register _____ is the control input.
(A) LOAD (C) serial input
(B) CLR (D) None of above
3. In bi-directional register data bit is shifted from left to right and right to _____.
(A) left (C) up
(B) right (D) None of above
4. An IC 74LS83 is a _____ bit parallel adder.
(A) four (C) one
(B) three (D) None of above
5. The Schmitt trigger has UTP and _____.
(A) MTP (C) NO- PT
(B) LTP (D) None of above



Q-2 List different types of Data transmission in registers and explain it with diagram. [05]

OR

Q-2 Draw the circuit of four bit serial shift register and explain it in detail. [05]

Q-3 Draw the circuit of four bit bidirectional shift register and explain it in brief. [05]

OR

Q-3 Explain Tri-state switch in detail. [05]

Q-4 Give an account of comparator. [05]

OR

Q-4 Draw a neat circuit of look ahead carry adder. [05]

Q-5 Explain CMOS to TTL interfacing in detail. [05]

OR

Q-5 Draw the diagram of Schmitt trigger as a interface circuit and explain it. [05]